

*Brought to you by ...*



**Priti Srinivas  
Sajja**

# Logic Circuits

**Professor**

*P G Department of Computer Science,  
Sardar Patel University, Vidyanagar-388 120, Gujarat, India.*

**PS01CMCA02**

**Course Content**

**Tutorial**

**Practice Material**

**Acknowledgement**

**References**

**Website**

**[pritisajja.info](http://pritisajja.info)**



# Topics

Basic gates and Universal gates  
Boolean algebra and Truth table  
Circuit Equivalence  
DeMorgan's Theorems



# Logic Gates

- Logic gates are the **fundamental building blocks** of digital systems.
- Gate is a logic circuit with **one or more inputs but only one output.**
- Gate is a logic circuit in which voltage levels represent logic 1 and logic 0.
- A table which contains **all possible alternatives** of input variables and corresponding output, is called a **truth table.**



# AND Gate

An **AND** gate has two or more input signals but only one output signal. **If all inputs are high then output is high.**


A	B	C	A AND B AND C(ABC)	
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



# OR Gate

An **OR** gate has two or more input signals but only one output signal. **If any input is high then output is high.**


A	B	C	A OR B OR C (A+B+C)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

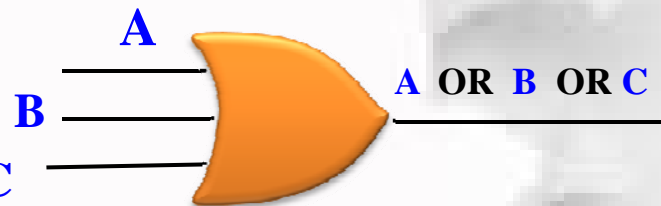

# NOT Gate

A **NOT** gate has one input signal and output signal complement to the input signal. **If the input is high then output is low.**


A	Complement A ( $\bar{A}$ )
0	1
1	0

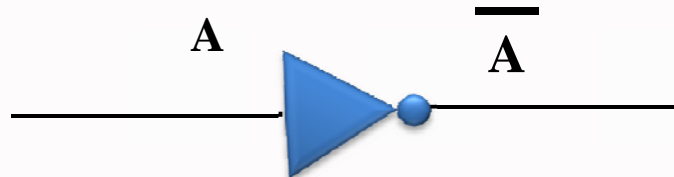

## NAND Gate

A **NAND** gate means **NOT** followed by **AND**.



A	B	A AND B(AB)	A NAND B( $\overline{AB}$ )
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

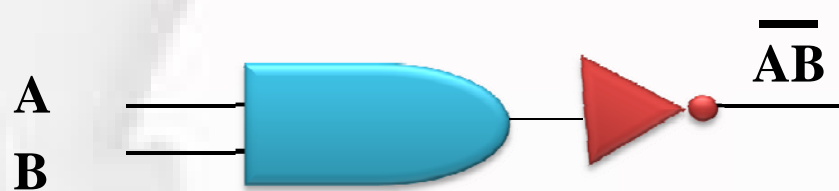

## NAND Gate

A **NAND** gate means **NOT** followed by **AND**.

A	B	A AND B(AB)	A NAND B(AB)
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0



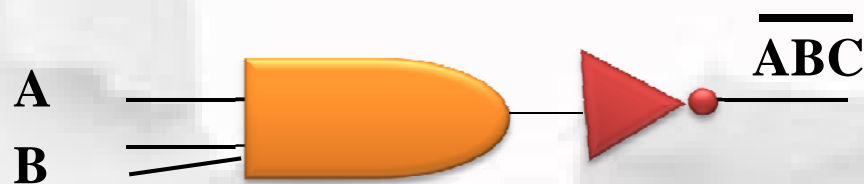
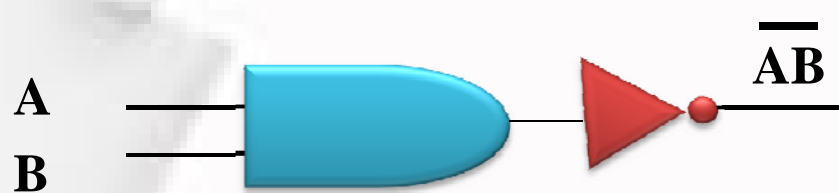





## NOR Gate

A **NOR** gate means **NOT** followed by **OR**.

A	B	A OR B(A+B)	A NOR B(A+B)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

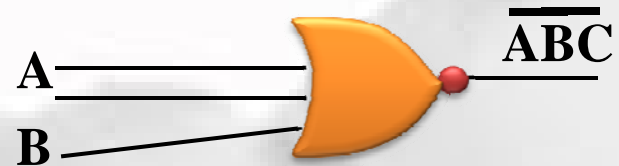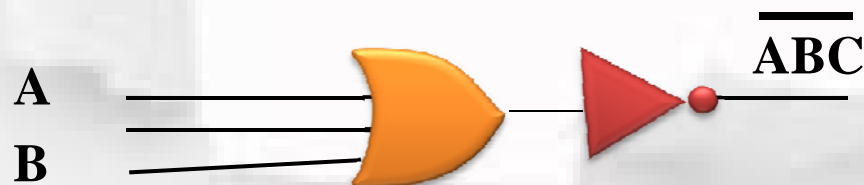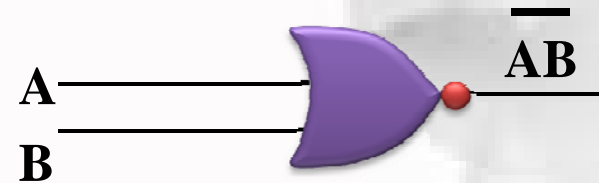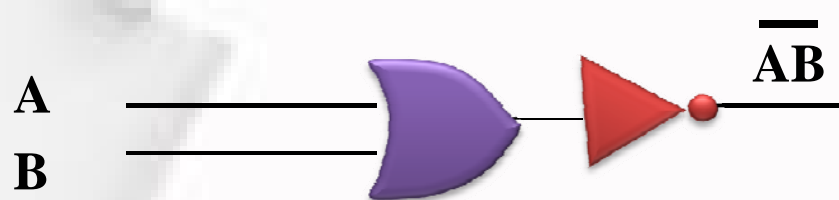

## Bubbled Gates

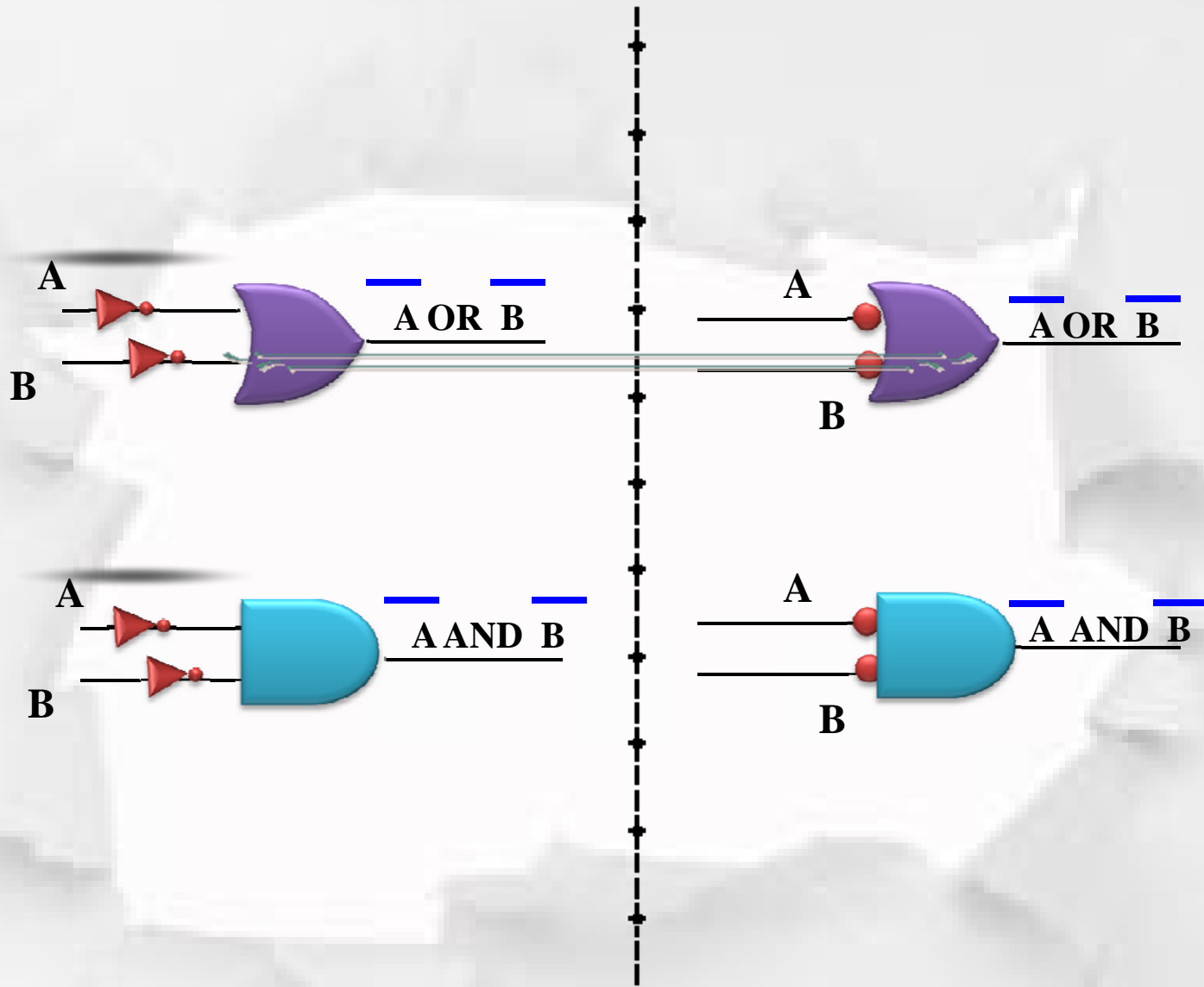


# NAND Gate


as NOT gate



as AND gate

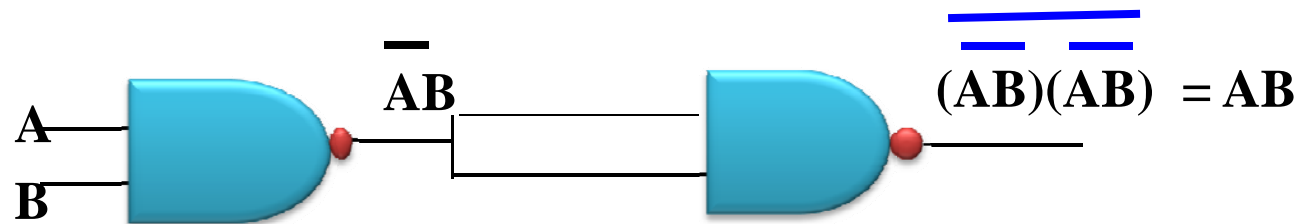


as OR gate

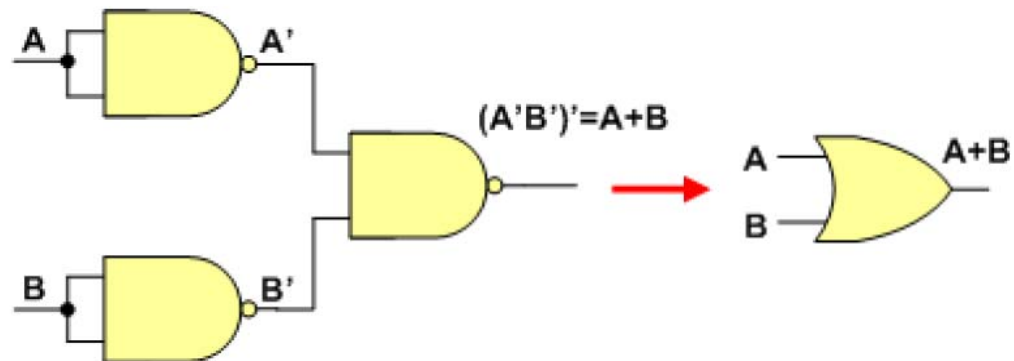


Universal Gate

# NOR Gate


as Not gate

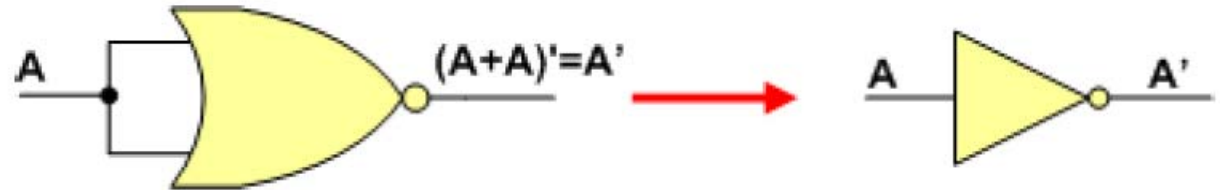

as OR gate

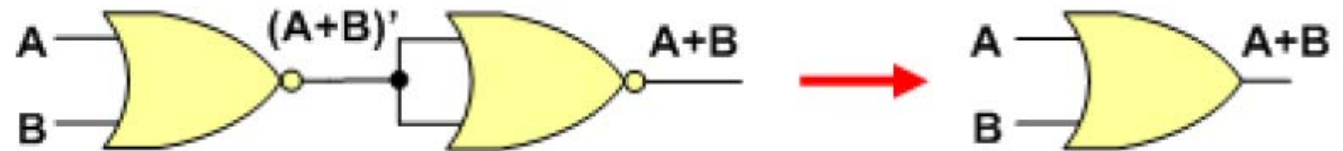

as AND gate

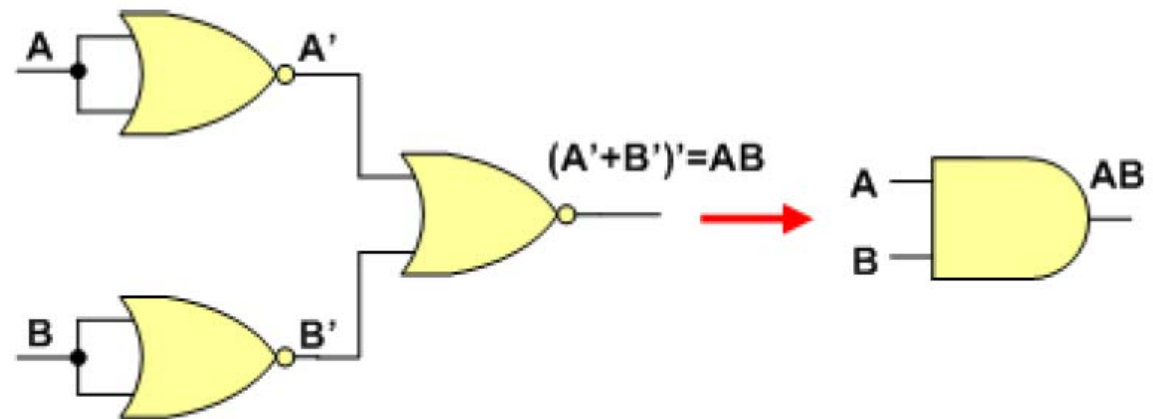



## Equivalent Gate/Circuits

A **NAND** gate is equivalent to an **inverted-input OR** gate.



An **AND** gate is equivalent to an **inverted-input NOR** gate.



## Equivalent Gate/Circuits

A **NOR** gate is equivalent to an **inverted-input AND** gate.



An **OR** gate is equivalent to an **inverted-input NAND** gate.




## Equivalent Gate/Circuits

Two NOT gates in series are same as a **buffer** because they cancel each other as  $A'' = A$ .




Implement  $F = XZ + Y'Z + X'YZ$

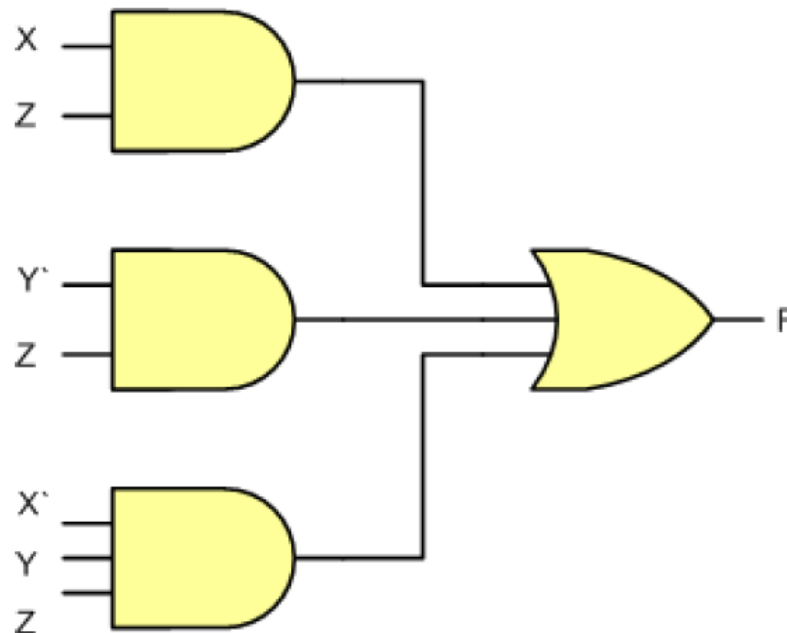


## Equivalent Gate/Circuits

Implement  $F = (X+Z) (Y'+Z) (X'+Y+Z)$

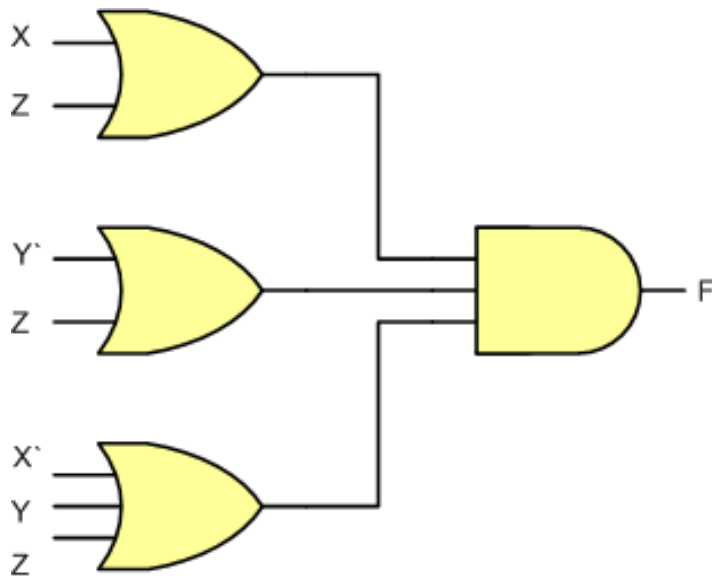

Implement  $F = (ZX + Y'Z + X'YZ)'$


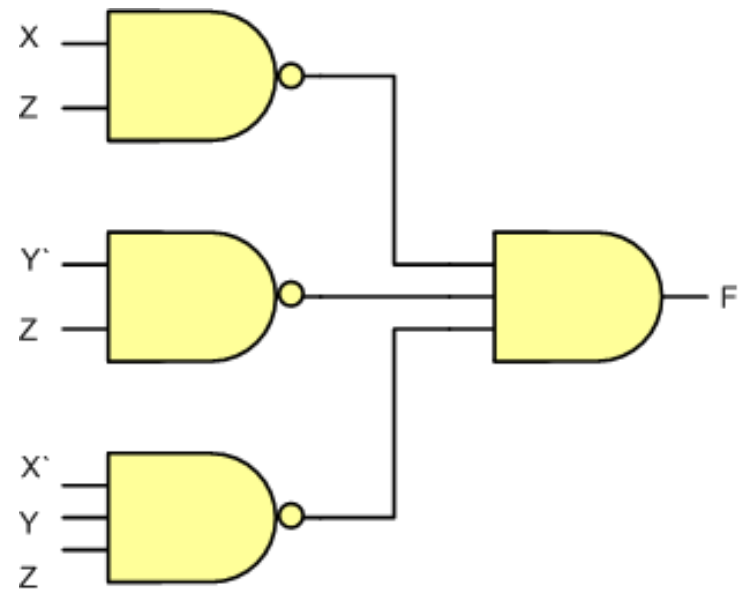




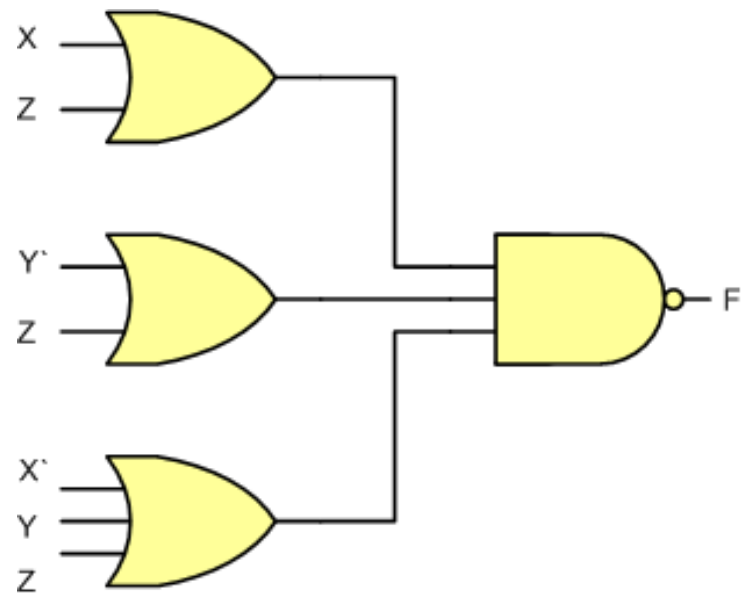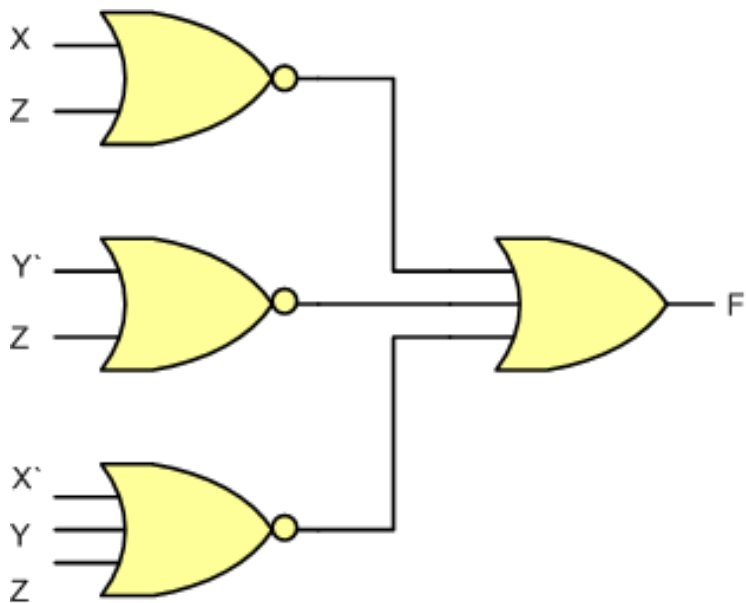
## Equivalent Gate/Circuits

$$F = \overline{(X + Z).(\bar{Y} + Z).(\bar{X} + Y + Z)} \text{ or}$$


$$\bar{F} = (X + Z)(\bar{Y} + Z)(\bar{X} + Y + Z)$$




# Decimal to Binary encoder

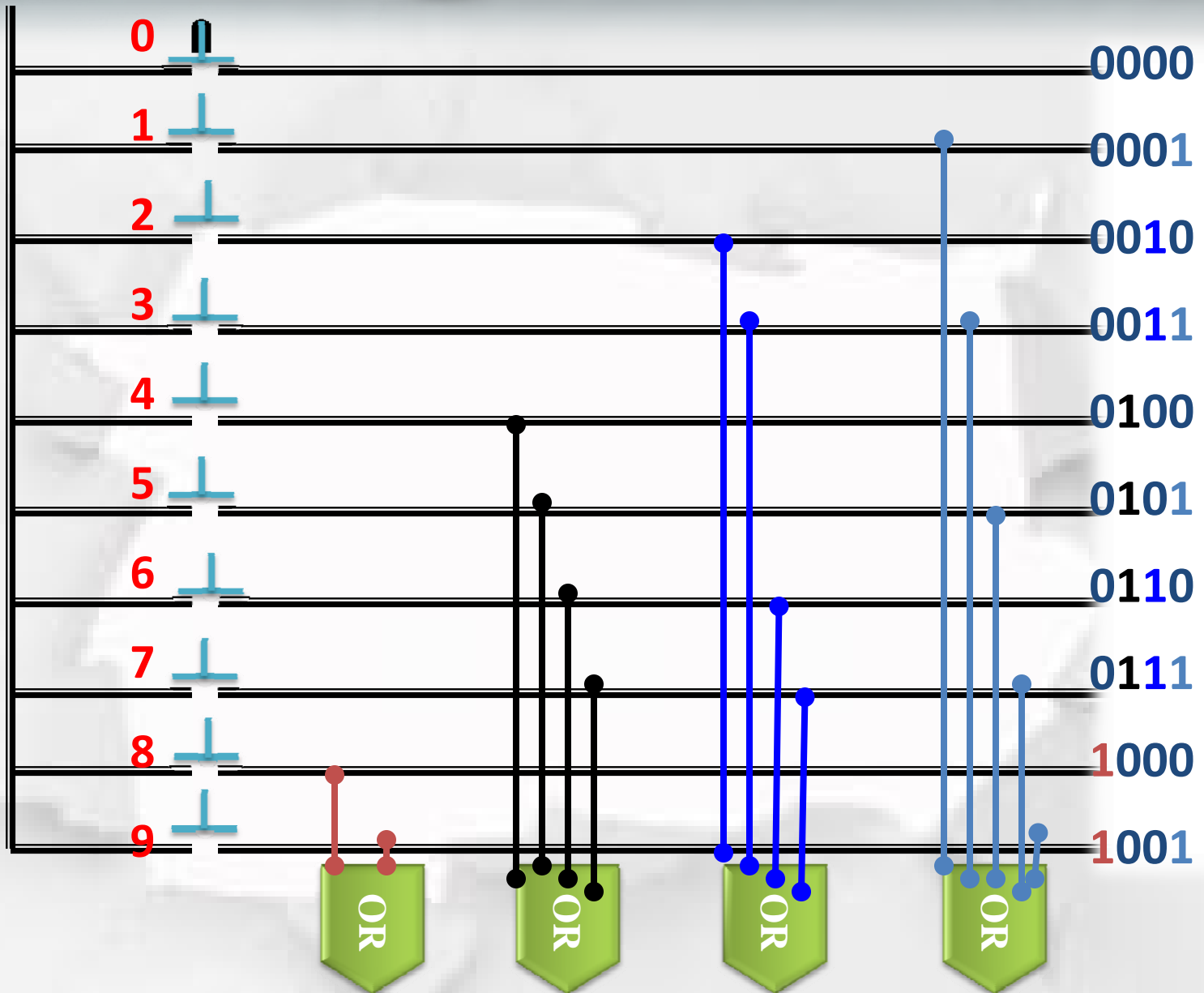

Block/Transmit 6 bit  
word

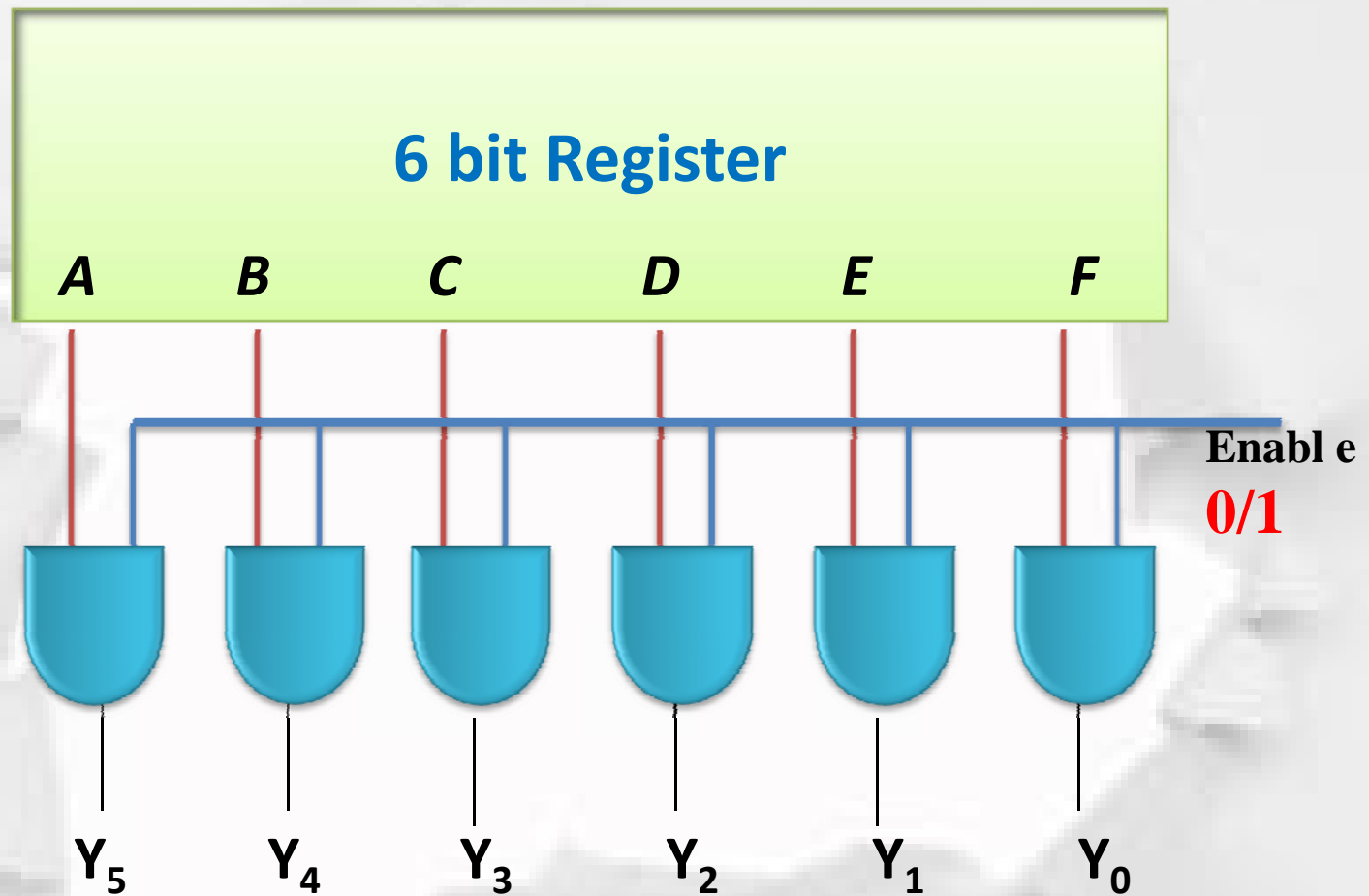


## 1 of 10 decoder

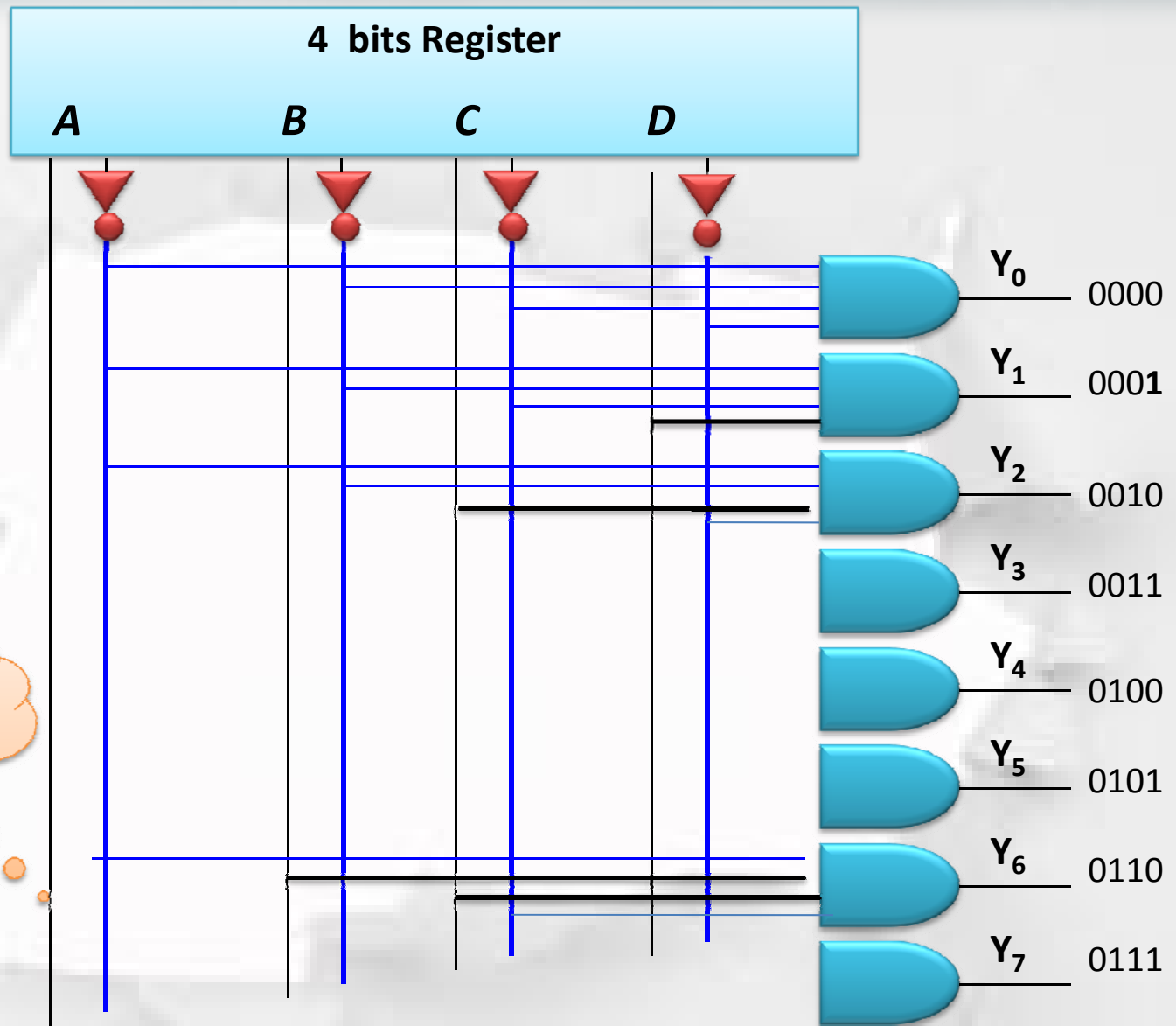



*Complete  
this...*



## 3 to 8 decoder

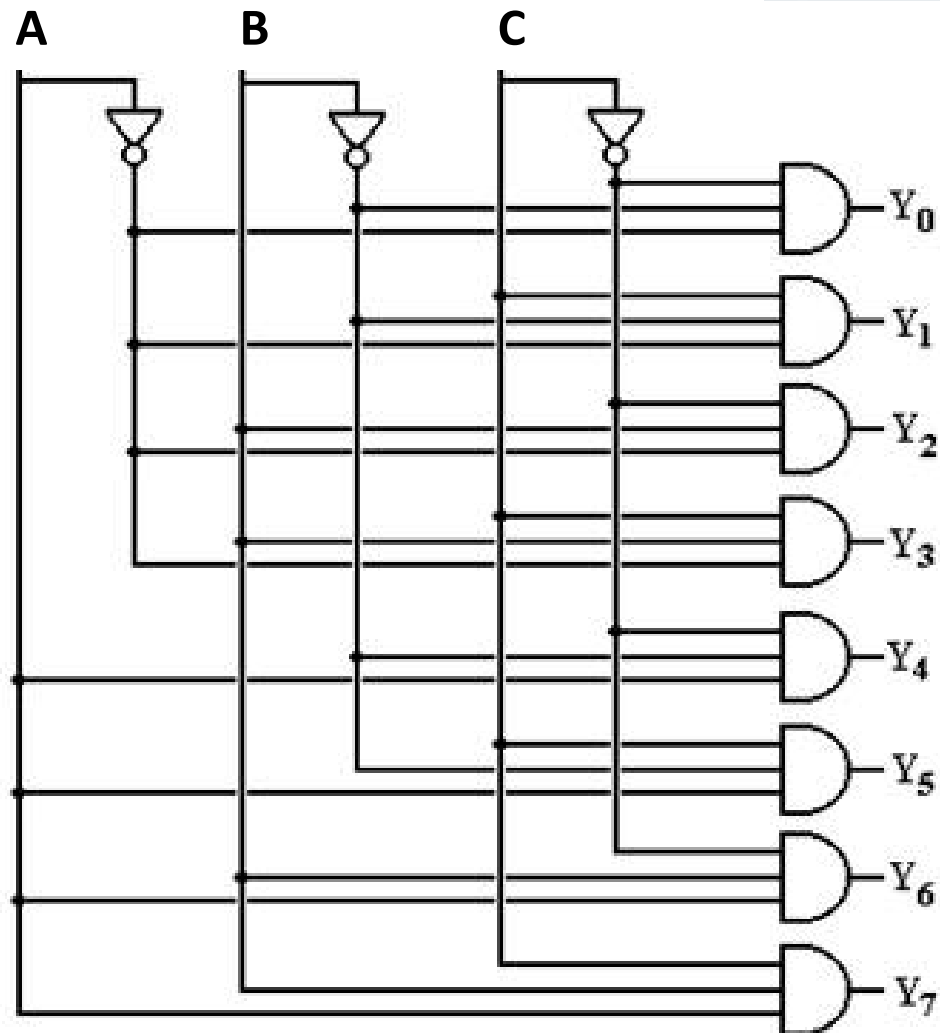


## 2 to 4 decoder

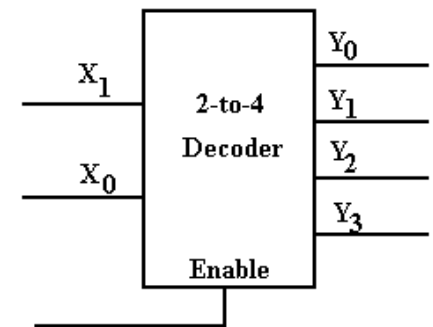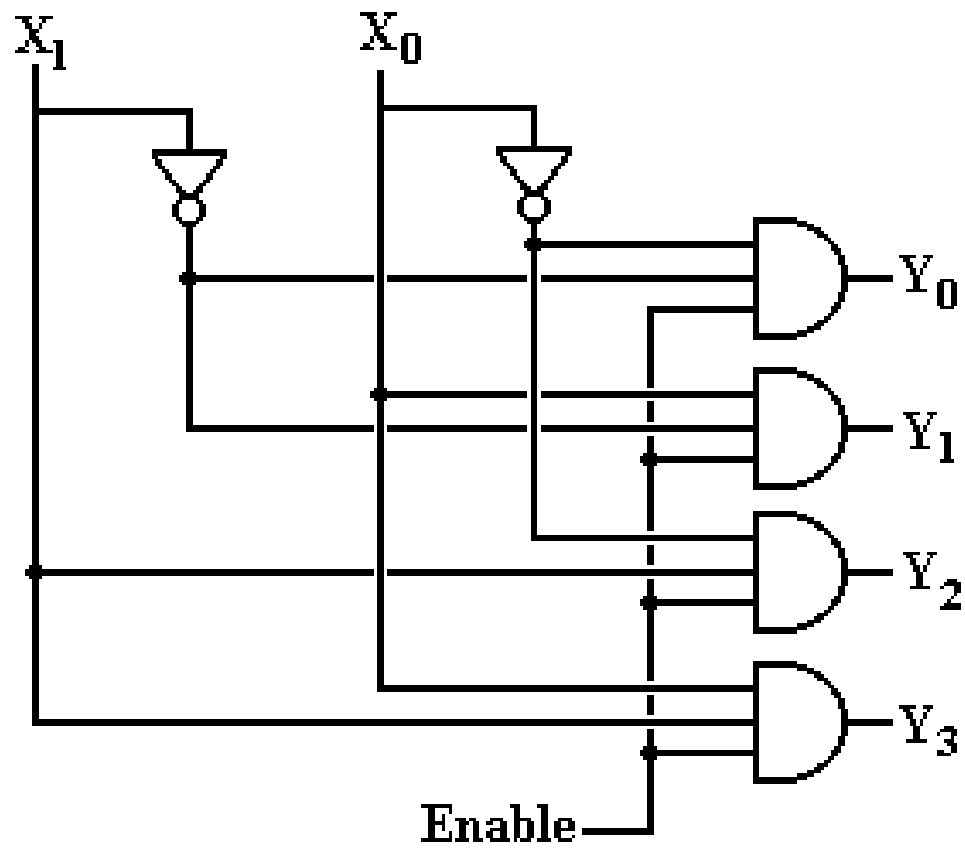


## XOR Gate

A	B	$\overline{A}B + A\overline{B}$	A XOR B ( $A \oplus B$ )
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

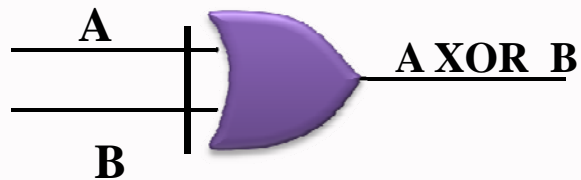
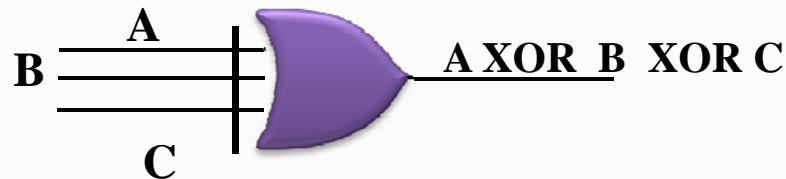
## XOR Gate

$$A \oplus B \oplus C = \overline{A} \overline{B} C + A \overline{B} \overline{C} + \overline{A} B \overline{C} + A B C$$




- Draw logic circuit and truth table for the same.
- If number of 1's are odd what will be the output?



## XOR Gate Applications

odd parity generator for a six bit word

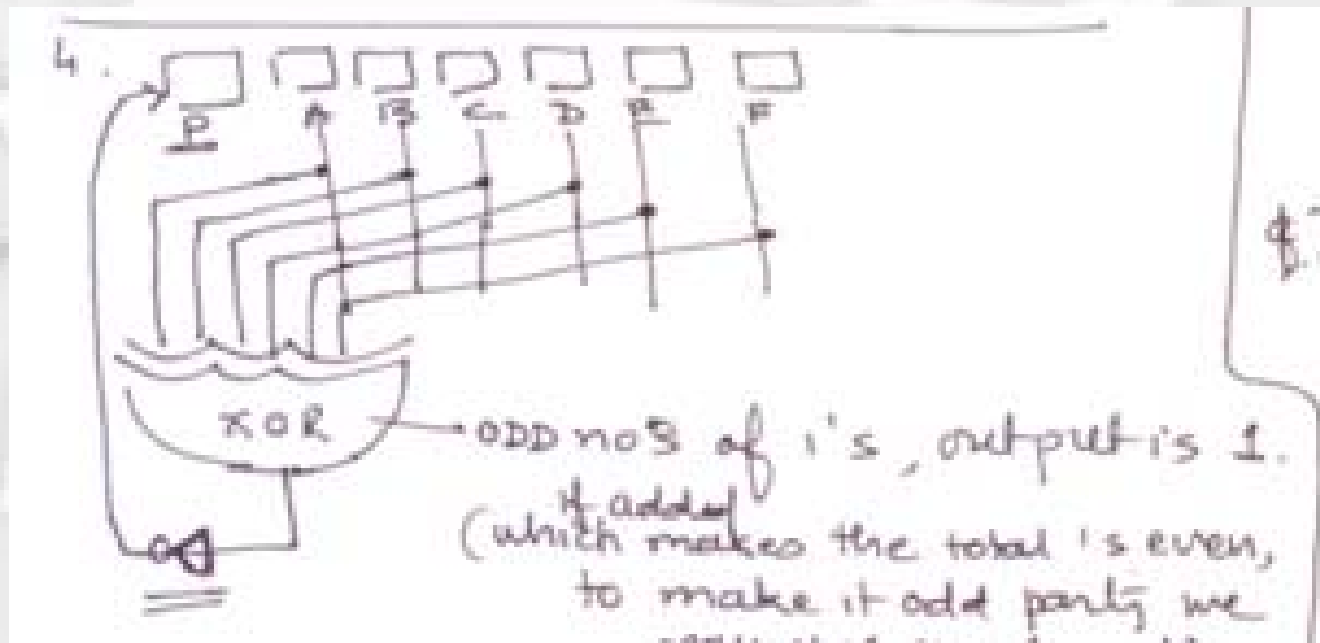

Can you draw odd parity tester for six bit word?

## Practice

Draw logic circuits for followings:

$$- \overline{A} \text{ OR } B \quad \text{or} \quad \overline{A + B}$$

$$- A \text{ OR } \overline{B}$$

$$- \overline{A} \text{ OR } \overline{B}$$

$$- \overline{A} \text{ AND } B \quad \text{or} \quad \overline{A} B$$

$$- A \text{ AND } \overline{B}$$

$$- \overline{A} \text{ AND } \overline{B}$$

Check  $\overline{A + B} = \overline{A} B$  using truth table.


# De Morgan's Theorem 1

- $\overline{A+B} = \overline{A} \overline{B}$
- Prove with help of truth table and draw logic circuits fro LHS and RHS.
- This can be extended for any number of variable eg.
- $\overline{A+B+C+D} = \overline{A} \overline{B} \overline{C} \overline{D}$
- $\overline{A+BC+DEF} = \overline{A} \overline{BC} \overline{DEF}$

## De Morgan's Theorem 2

- $\overline{AB} = \overline{A} + \overline{B}$
- Prove with help of truth table and draw logic circuits fro LHS and RHS.
- This can be extended for any number of variable eg.
- $\overline{A B C D} = \overline{A} + \overline{B} + \overline{C} + \overline{D}$
- $\overline{(A) (BC) (DEF)} = \overline{(A)} + \overline{(BC)} + \overline{(DEF)}$

## Realization of AND using NAND

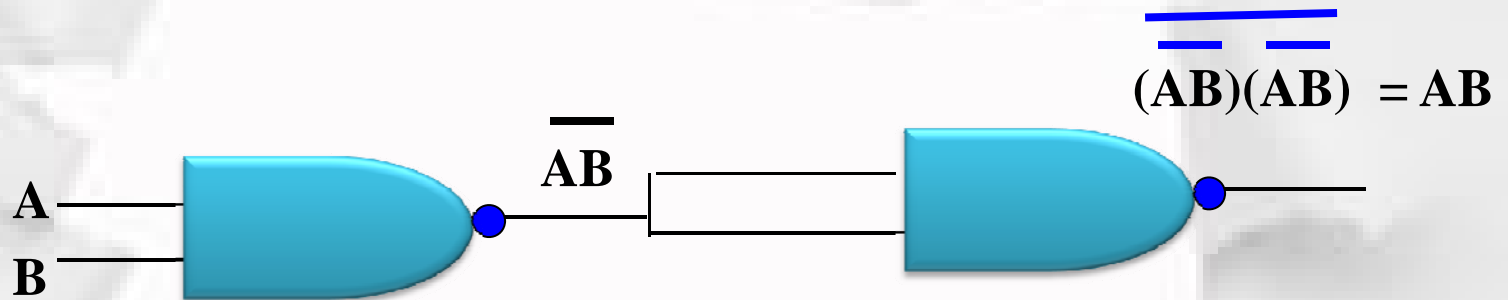

- Try to realize OR gate and NOT gate using NAND gate
- Try to realize AND, OR gate and NOT gate using NOR gate



# Boolean Relations

- Commutative Law:

- $A+B=B+A$

- $AB=BA$

- Associative Law:

- $A+(B+C) = (A+B) +C$

- $A(BC) = (AB)C$

- Distributive Law:

- $A(B+C)=AB+AC$

## Boolean Relations

- $A+0=A$
- $A+A=A$
- $A+1=1$
- $A+\bar{A}=1$
- $A0=0$
- $AA=A$
- $A1=A$
- $A\bar{A}=0$

$$\bar{\bar{A}} = A$$

**Prove that  $A+BC=(A+B)(A+C)$**

- **RHS=**
- **$(A+B)(A+C)$**
- **$AA + AC + AB + BC$**
- **$A + AC + AB + BC$**
- **$A(1+C+B) + BC$**  (adding 1 into anything is 1)
- **$A(1) + BC$**
- **$A+BC$**
- **=LHS**

**Prove that  $A(B+C)=AB+AC$  with help of truth table**

A	B	C	B+C	$A(B+C)$	AB	AC	$AB+AC$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1