

PID: \_\_\_\_\_ Name: \_\_\_\_\_ Marks: \_\_\_\_\_/30

- Design a logic circuit that
  - considers a six bit words and passes if a positive signal is given
  - inverts a six bits word from an input register into an output register.
  - acts as a controlled inverter.
- Draw 1 to 10 decoder using AND gates.
- Complete following truth table. From the truth table find out equation. Also draw equivalent logic circuit for the same.

A	B	C	$X = ABC$	$Y = AB'C'$	$Z = A'B'C$	$L = A'BC'$	$X+Y+Z+L$
0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	1
0	1	0	0	0	0	1	1
0	1	1	0	0	0	0	0
1	0	0	0	1	0	0	1
1	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0
1	1	1	1	0	0	0	1

- Consider the truth table find out equation represented by X. Also draw equivalent logic circuit for the same.

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Draw logic circuit of 2's complement adder subtractor. Also state objective of this circuit diagram.
- Define latch. Give circuit diagram of a SR latch with truth table.
- Draw circuit diagram of a buffer register. Define how may flip-flops are needed to construct a register capable of storing a byte?
- What is a counter? Draw circuit of a ring counter.

-----XXX---XX---XXX-----

